
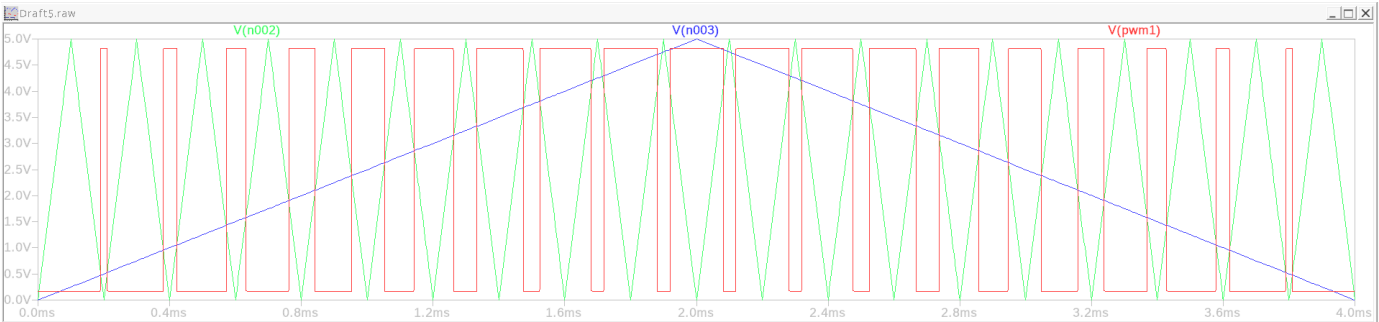





Assignment 5 - Bridge DC-DC converters

Forjanic Rémy (511448)


Question 1 - Control of DC-DC converters: Single PWM

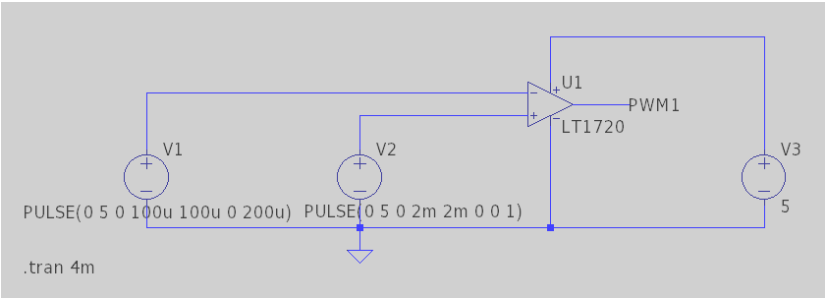

Question 2 - Control of DC-DC converters: Dual PWM

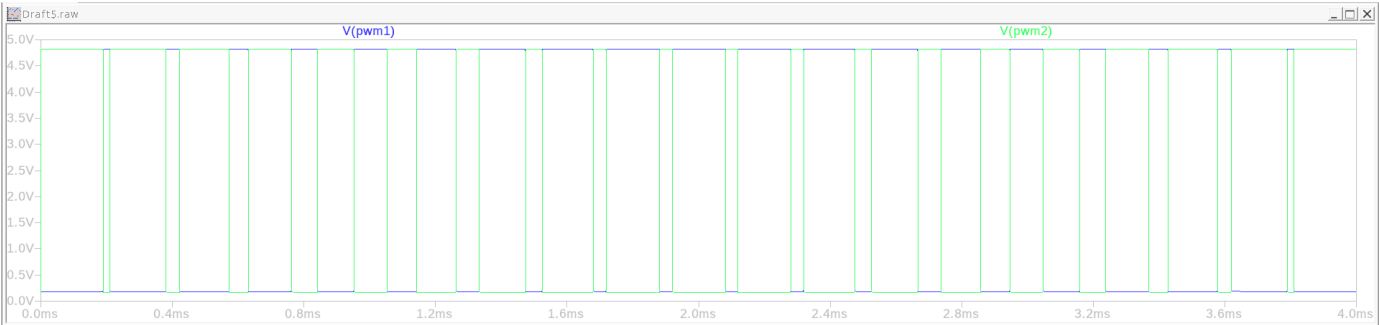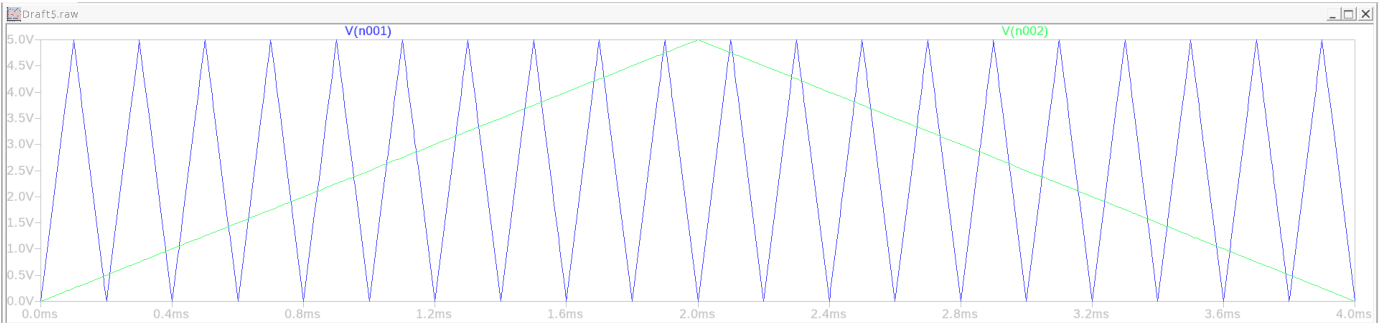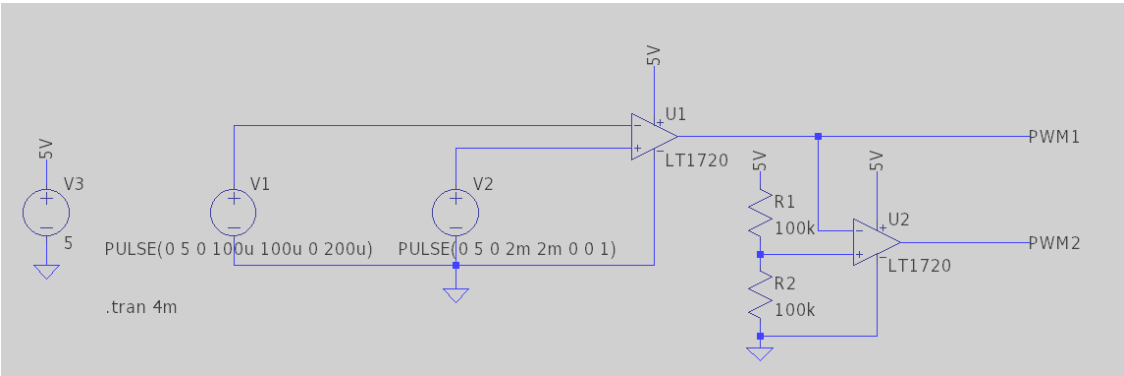

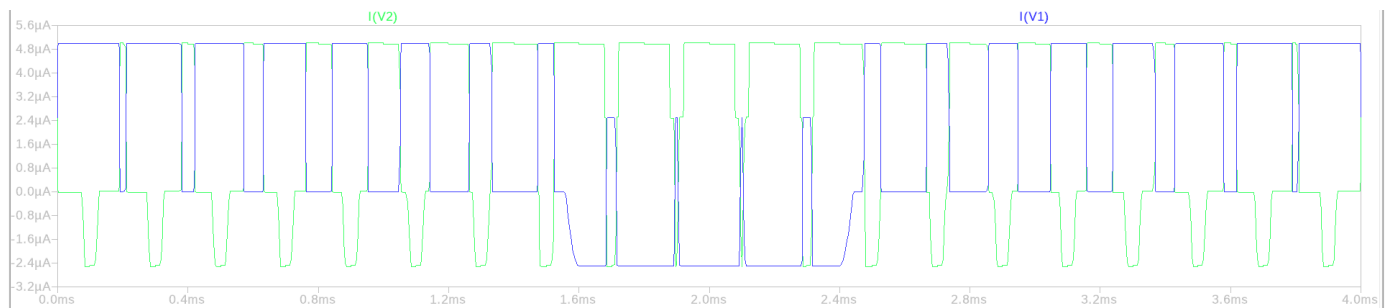
Question 3 - Control of DC-DC converters: Dual PWM with dead time




Verify the calculated dead time with the simulation results.




Show in a simulation the voltage across and current through the RL load.

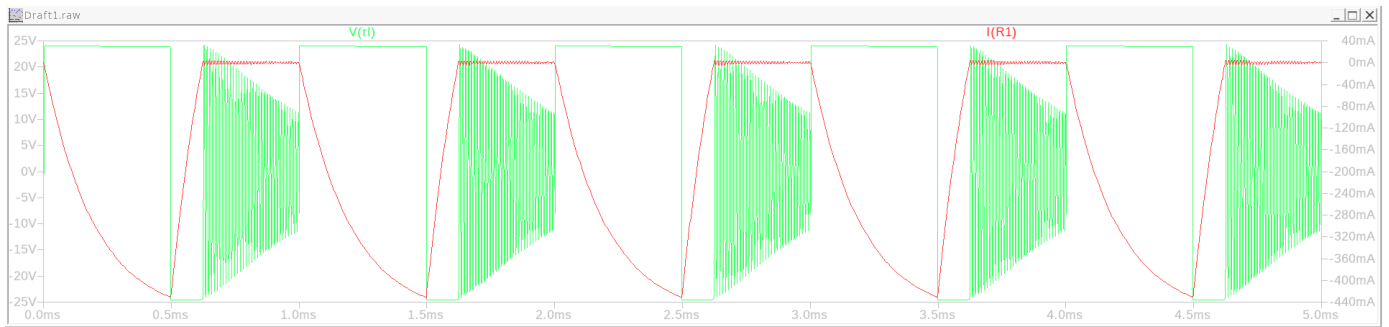

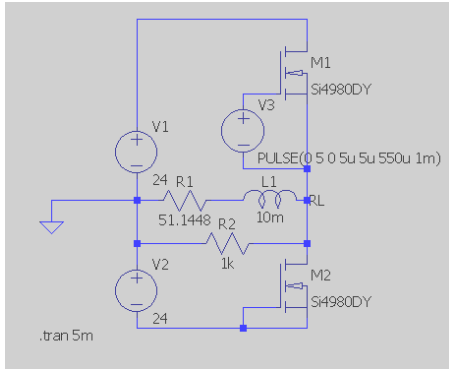Question 5 - Unipolar switching of a RL load with bleeding resistor across the load




$D = 0.55$

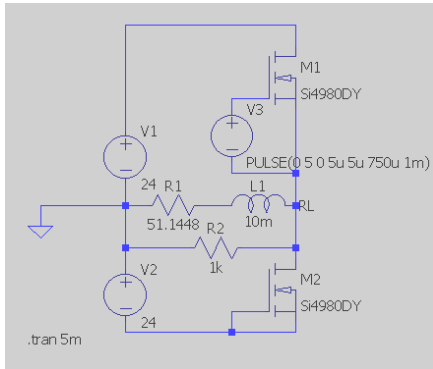


$D = 0.75$

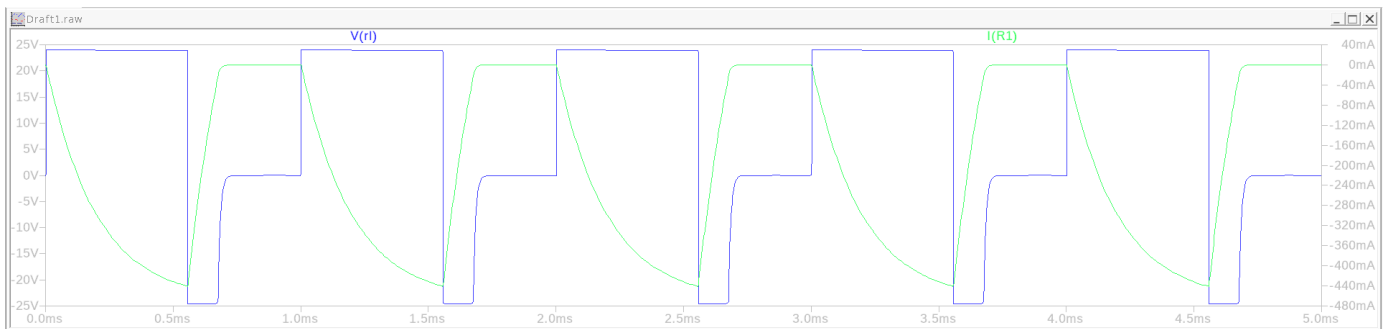Show in a simulation the voltage across and current through the RL load.




$D = 0.55$

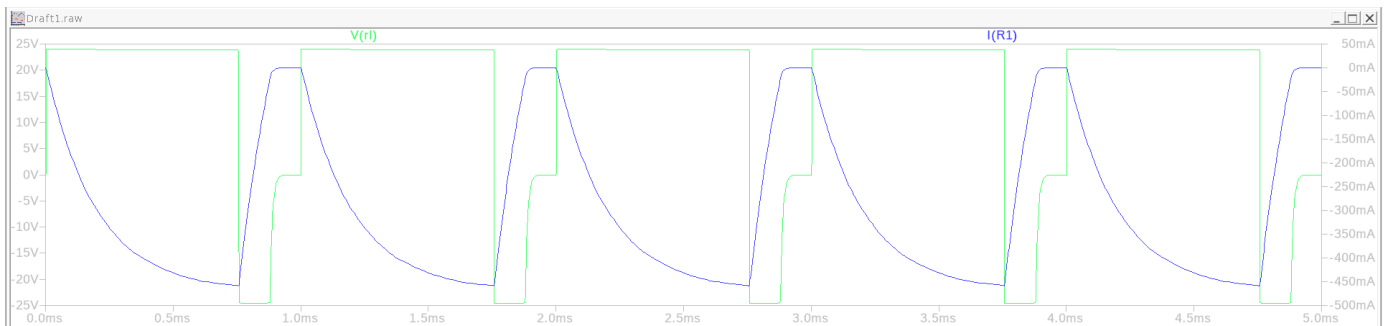


$D = 0.75$

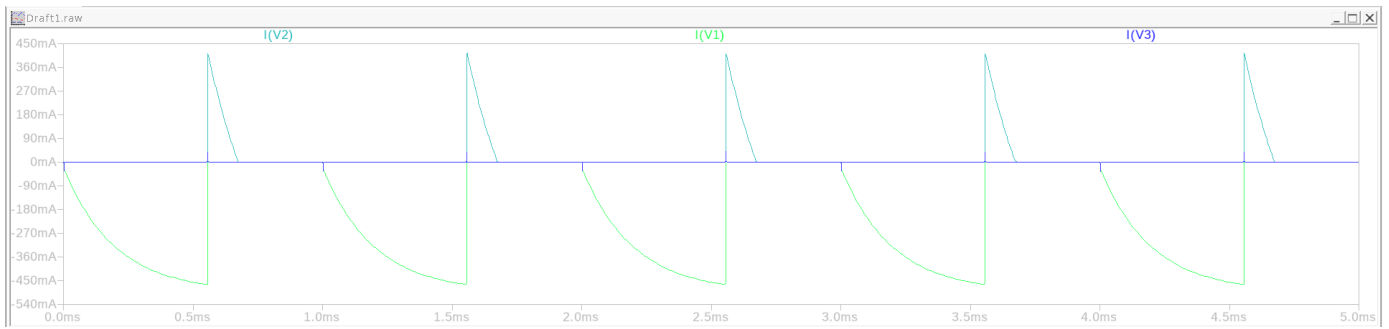Show in a simulation the source currents.




$D = 0.55$

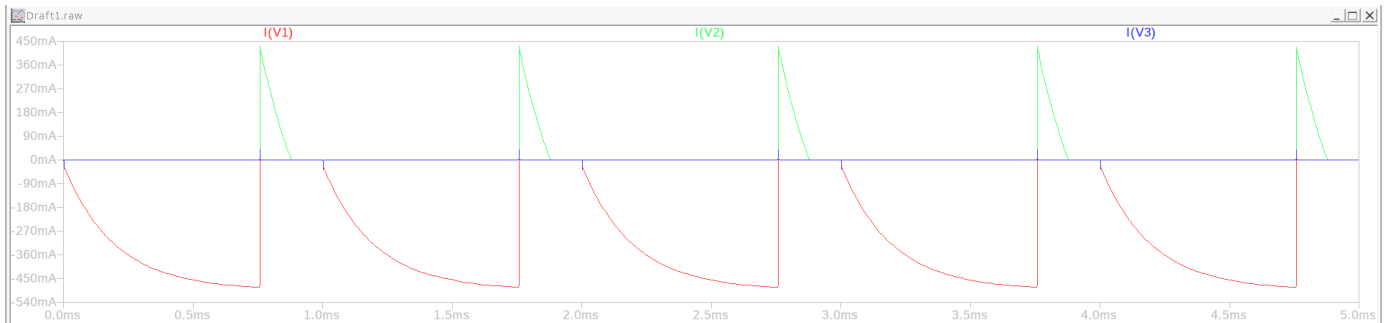


$D = 0.75$

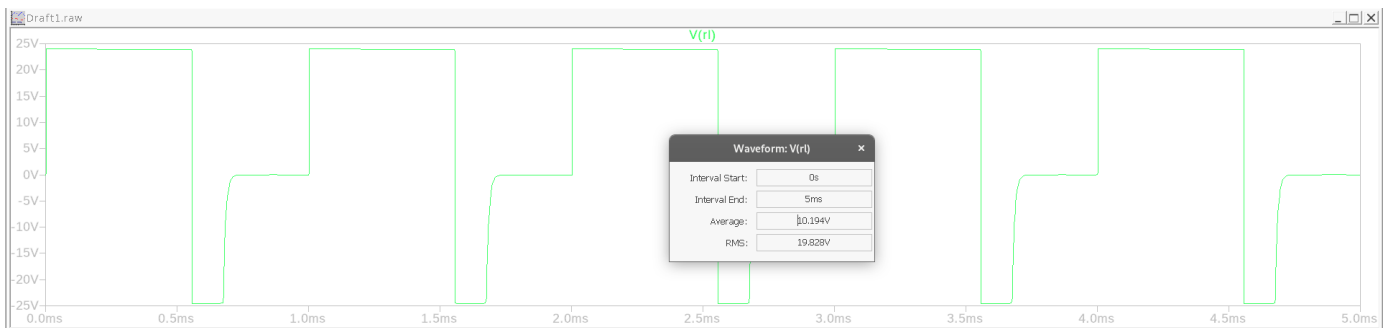What is the average voltage across the RL load?




$D = 0.55$

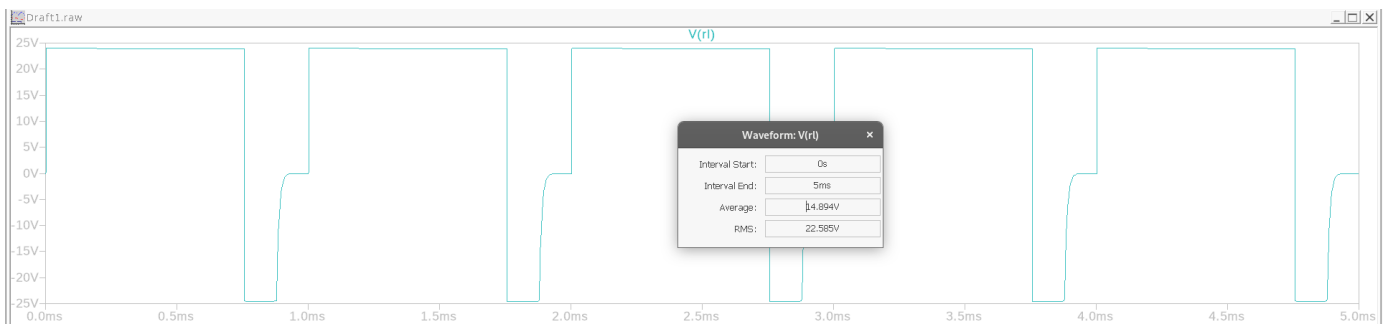


$D = 0.75$

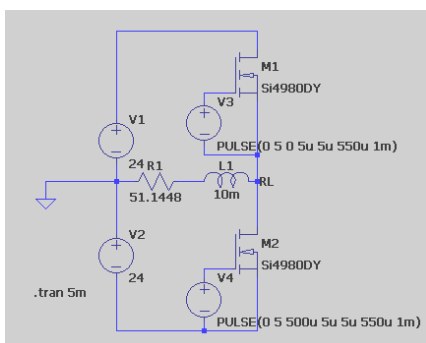Question 6 - Bipolar switching RL load


$$R1 = \frac{511448}{10000} = 51.1448\Omega$$



$D = 0.55$

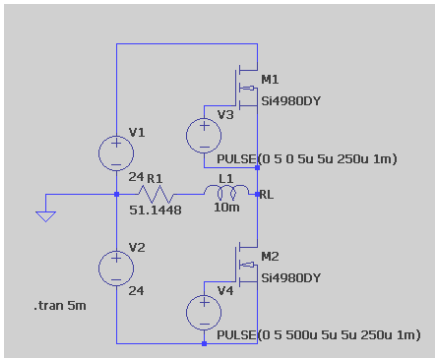


$D = 0.25$

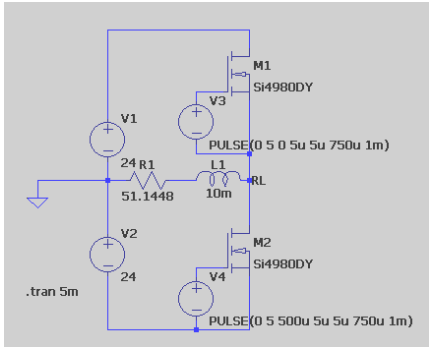


$D = 0.75$

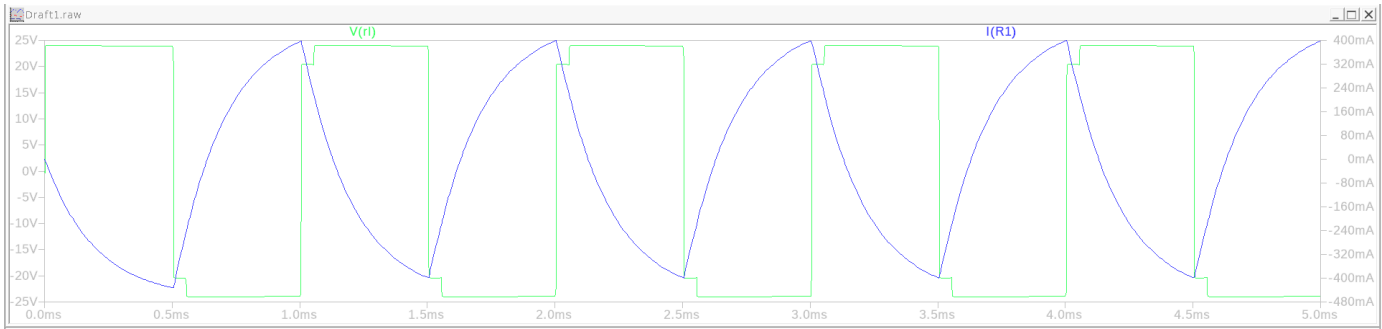
Show in a simulation the voltage across and current through the RL load.



$D = 0.55$

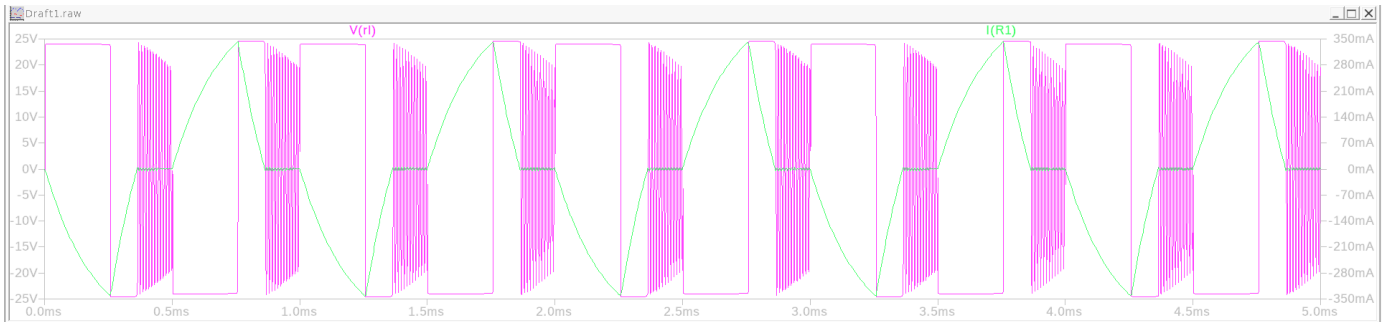


$D = 0.25$

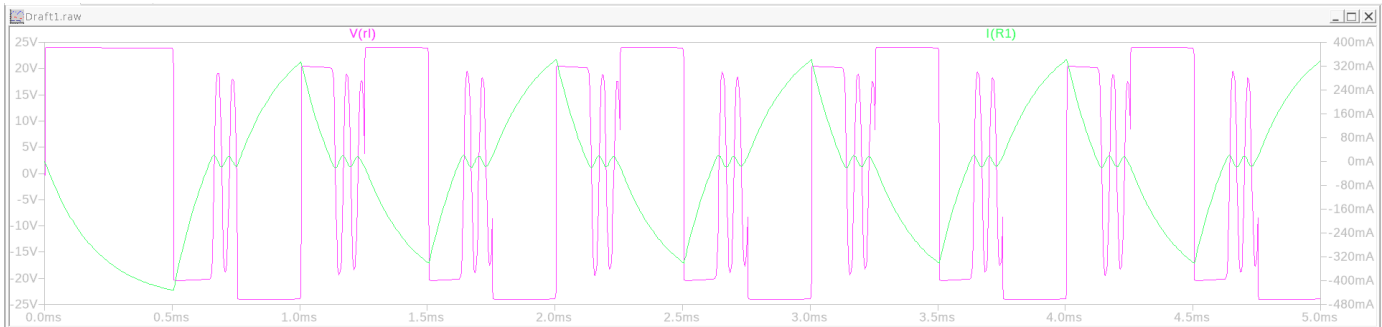


$D = 0.75$

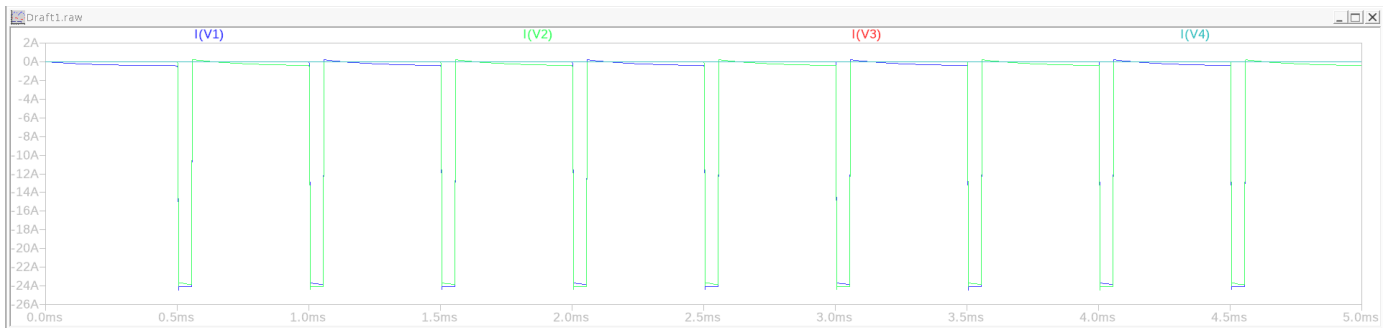
Show in a simulation the source currents.



$D = 0.55$

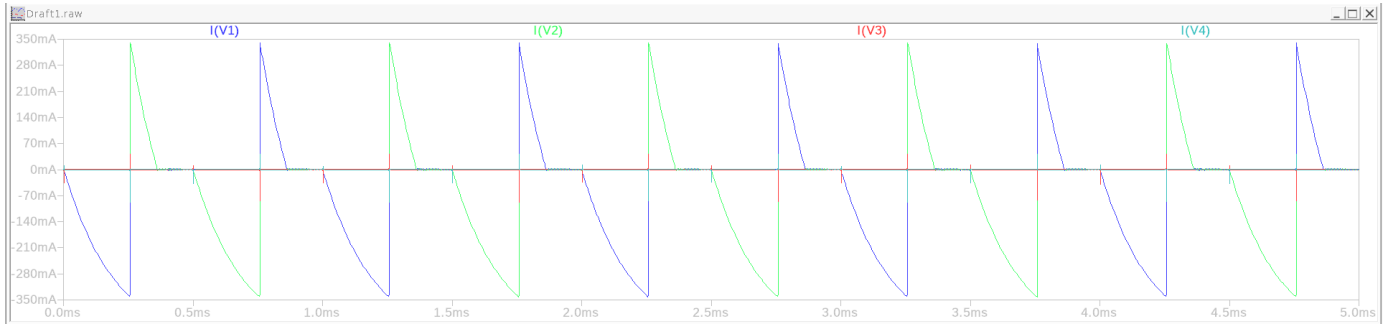

$D = 0.25$

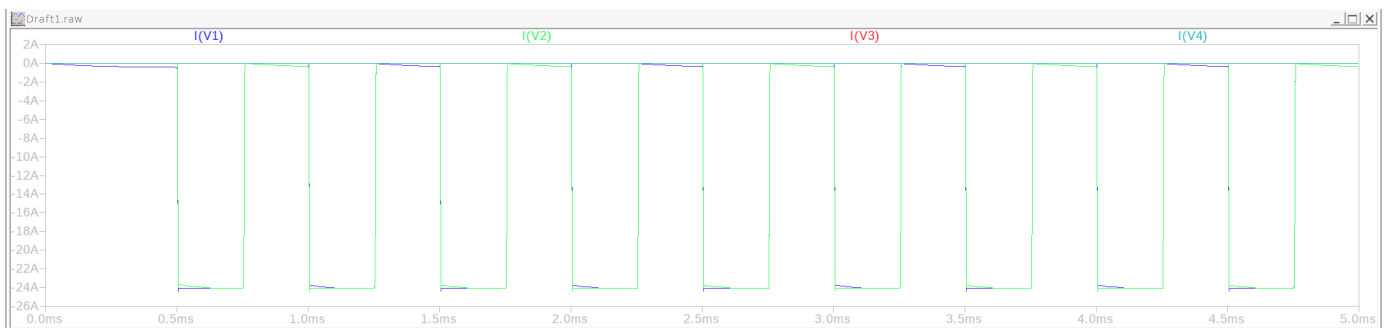


$D = 0.75$


What is the average voltage across the RL load?



$D = 0.55$

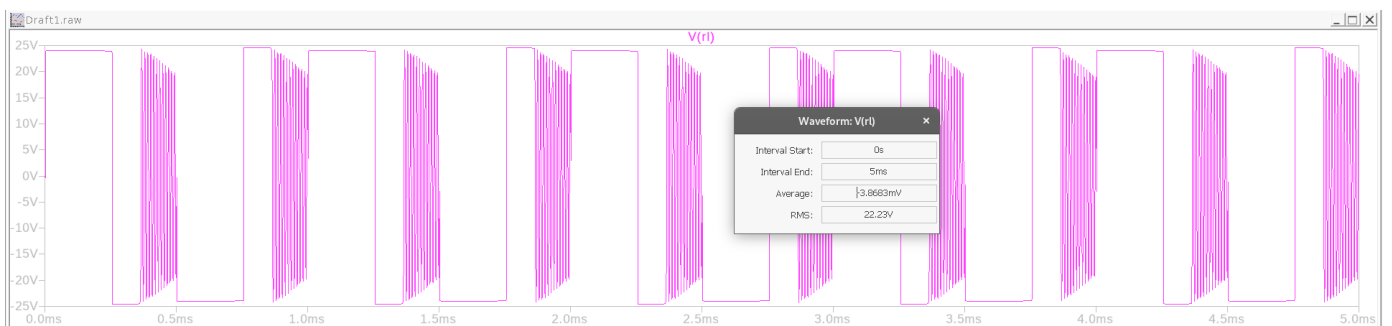


$D = 0.25$

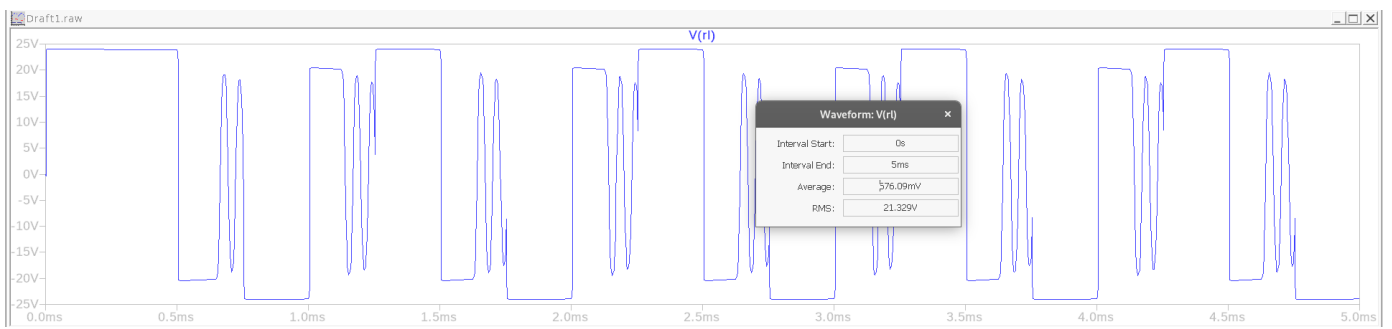


$D = 0.75$

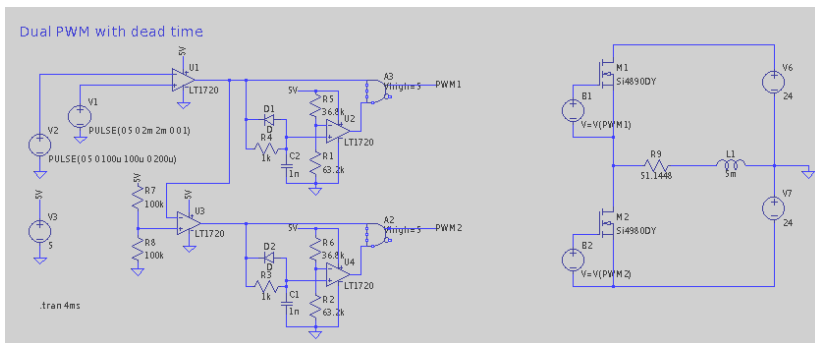Question 7 - PWM for half bridge


$$R1 = \frac{511448}{10000} = 51.1448\Omega$$



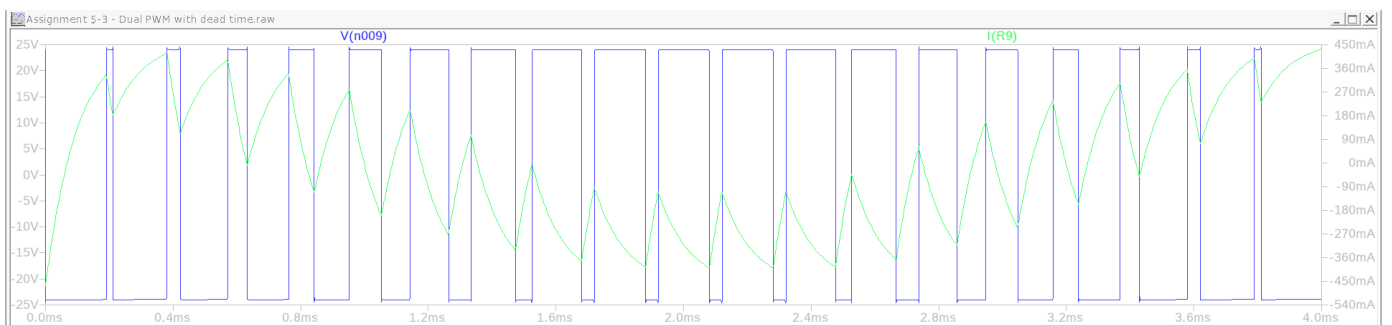Show in a simulation the voltage across and current through the RL load.



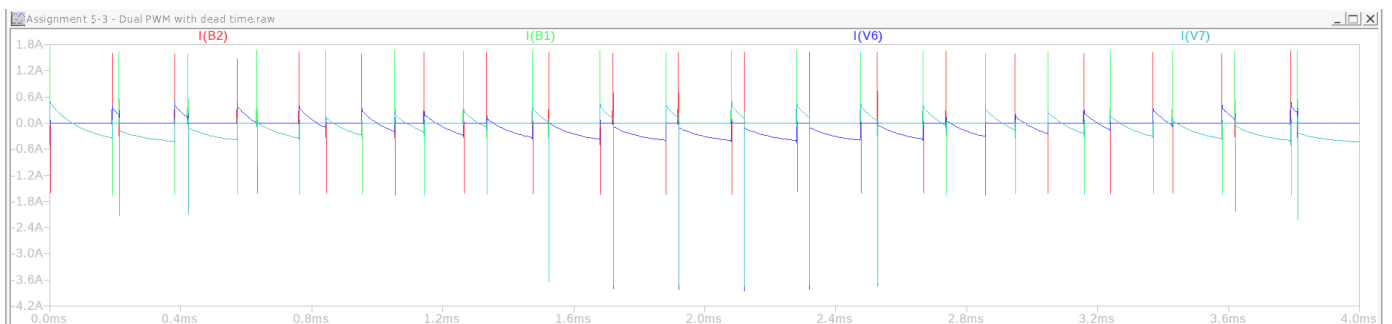Show in a simulation the source currents.



What is the average voltage across the RL load?.

