
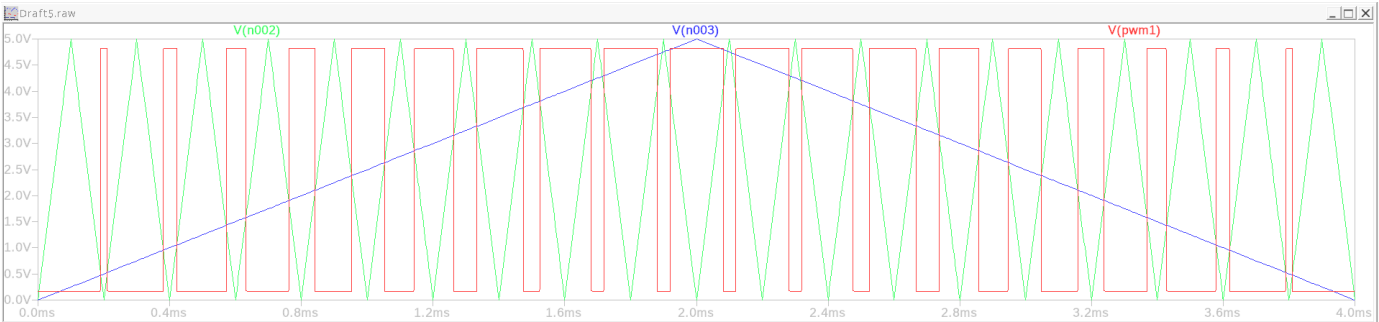





Assignment 5 - Bridge DC-DC converters

Forjanic Rémy (511448)


Question 1 - Control of DC-DC converters: Single PWM

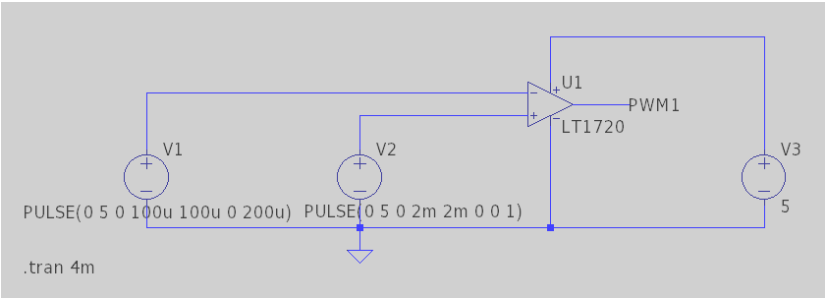

Question 2 - Control of DC-DC converters: Dual PWM

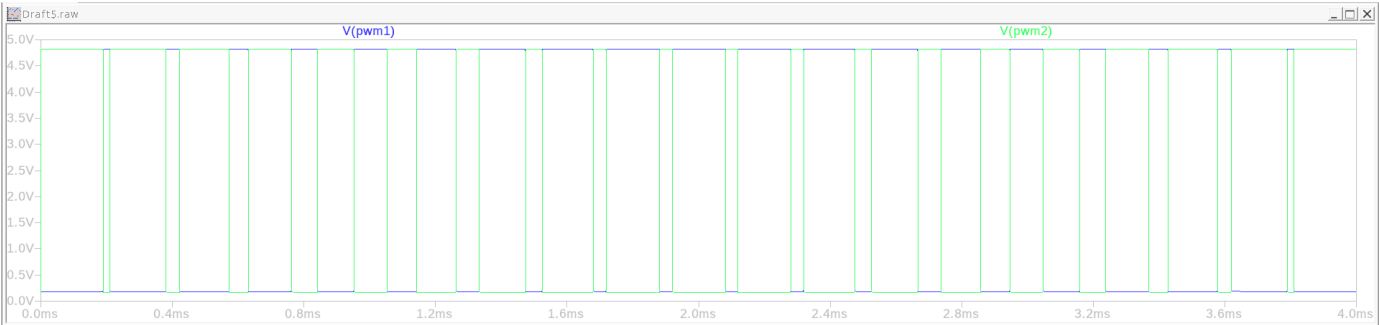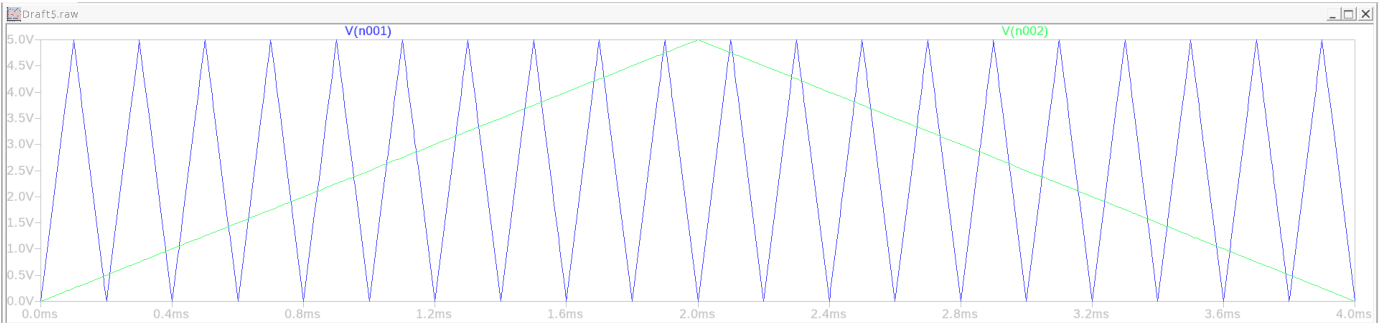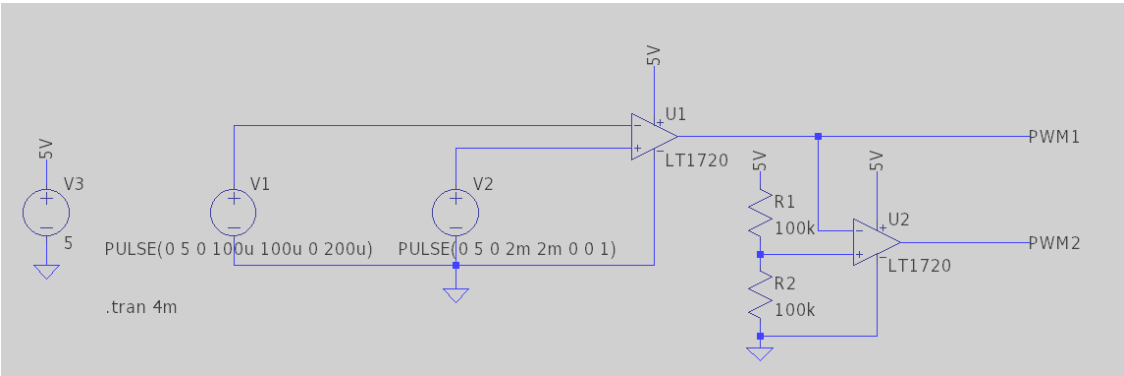

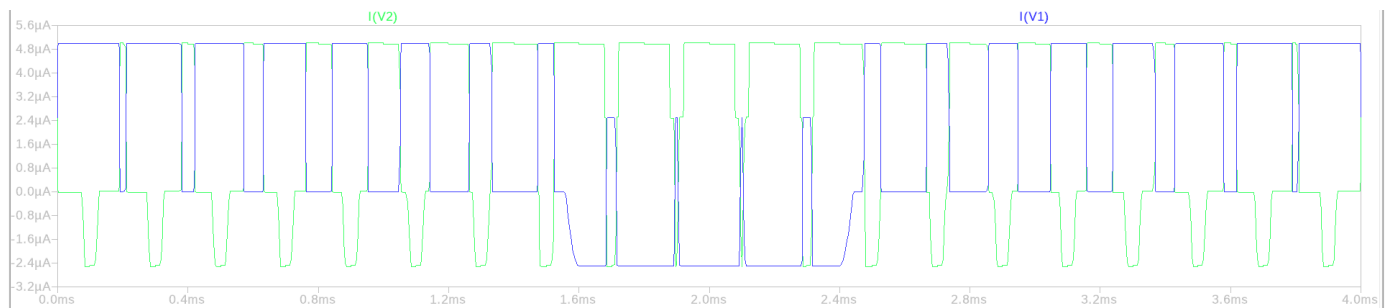
Question 3 - Control of DC-DC converters: Dual PWM with dead time



Since $R_4 = R_3$ and $C_1 = C_2$: $t_{\Delta} = R_3 \times C_1 = 1k \times 1n = 1\mu s$


Verify the calculated dead time with the simulation results.



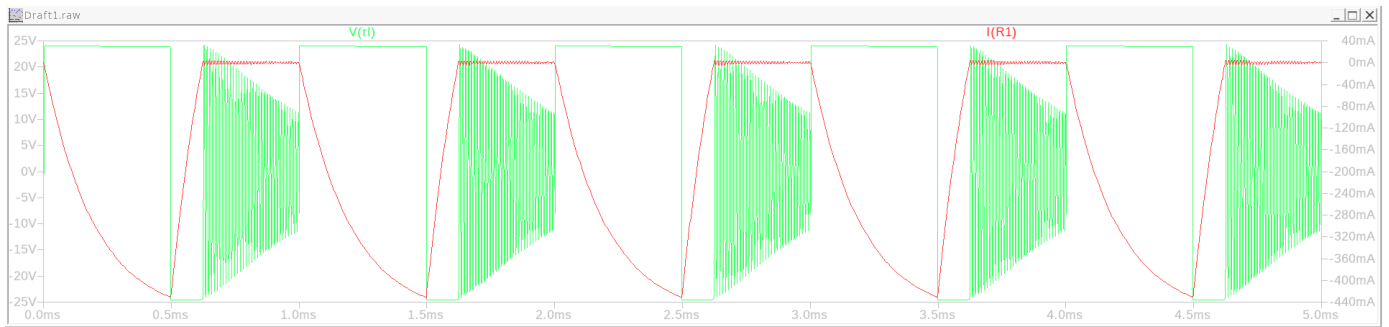


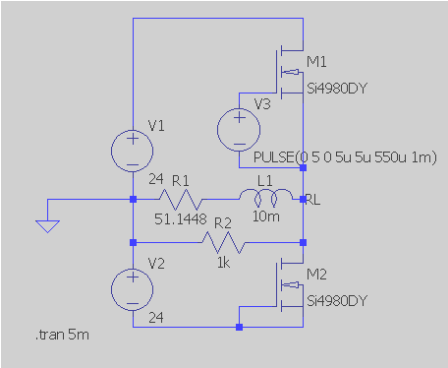Question 5 - Unipolar switching of a RL load with bleeding resistor across the load

I don't understand why it's saying the duty cycle is 0.55 and not 0.5 even though the period, the rise time, the on time and the fall time hasn't been changed.




$D = 0.5$

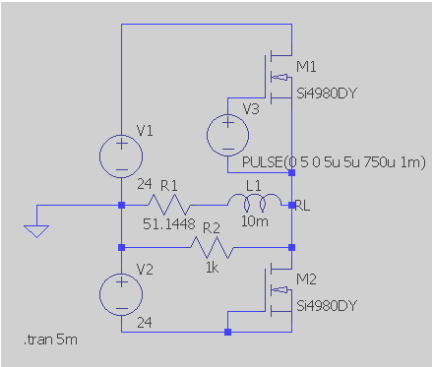


$D = 0.75$

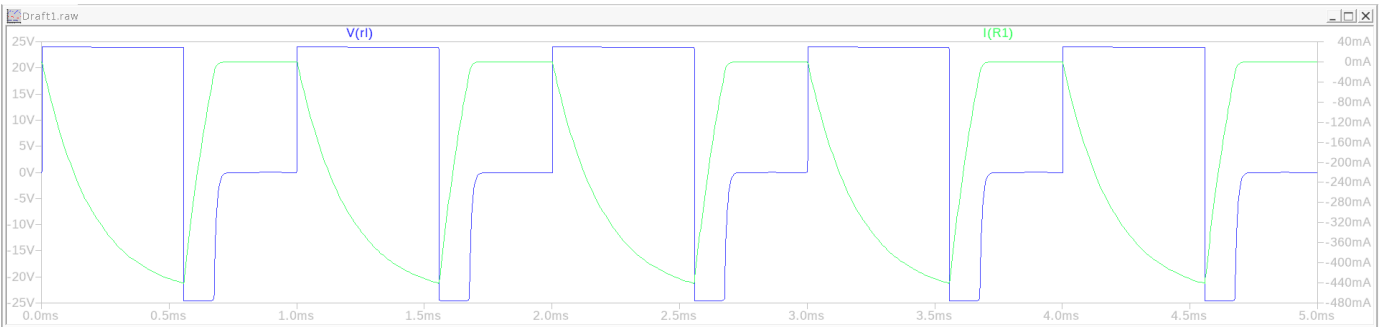Show in a simulation the voltage across and current through the RL load.




$D = 0.55$

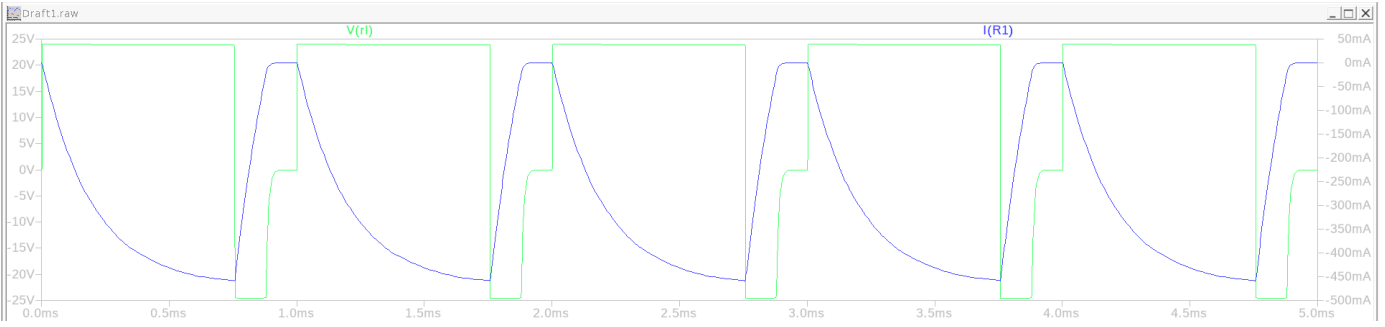


$D = 0.75$

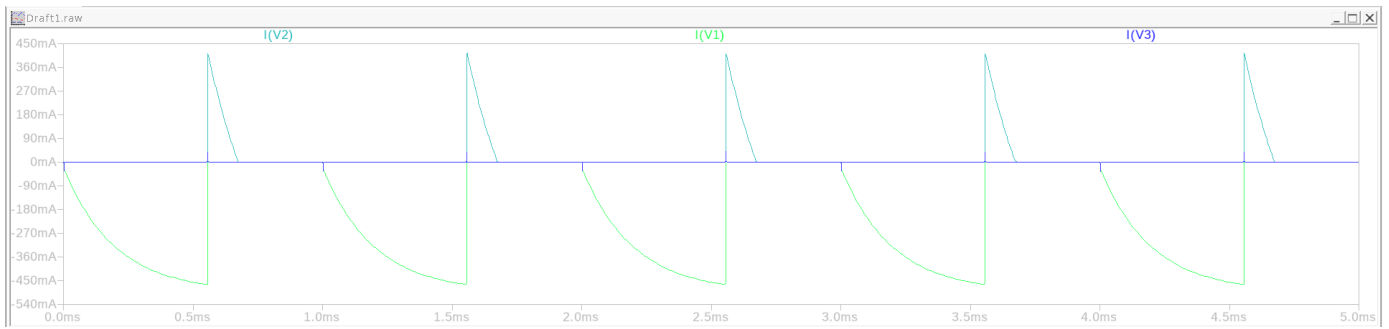Show in a simulation the source currents.




$D = 0.55$

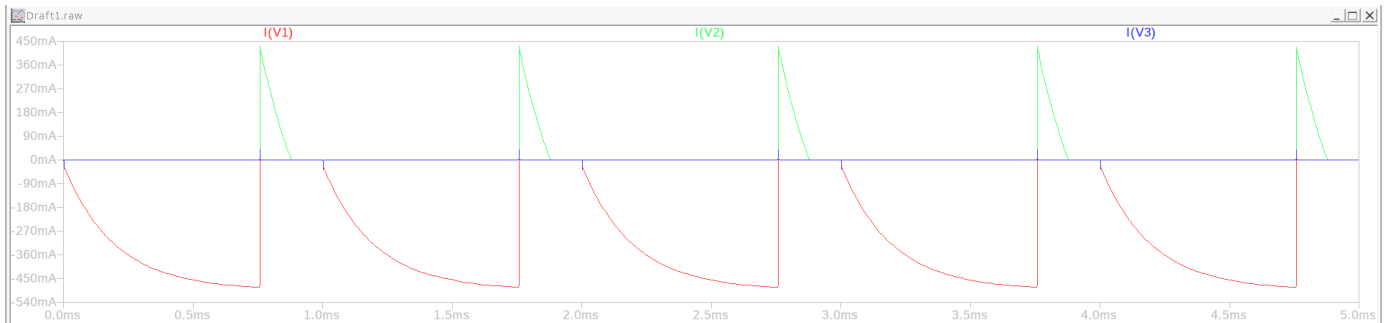


$D = 0.75$

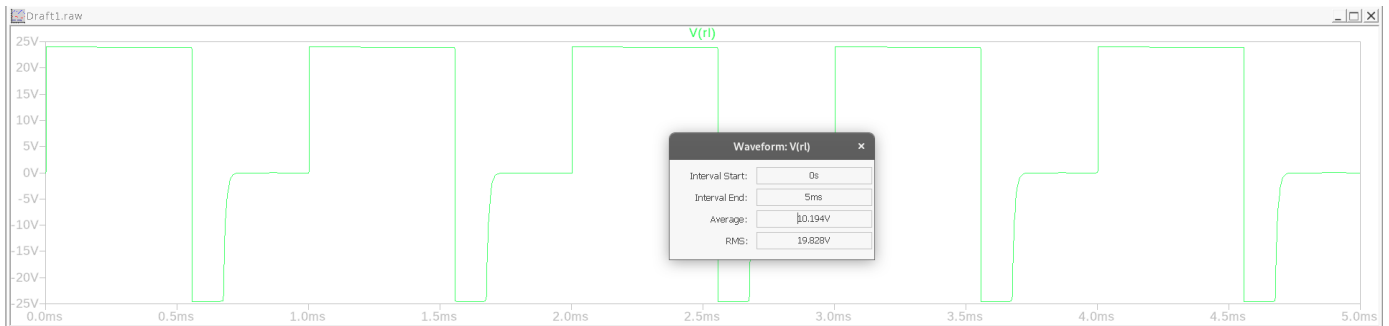What is the average voltage across the RL load?



$D = 0.55$

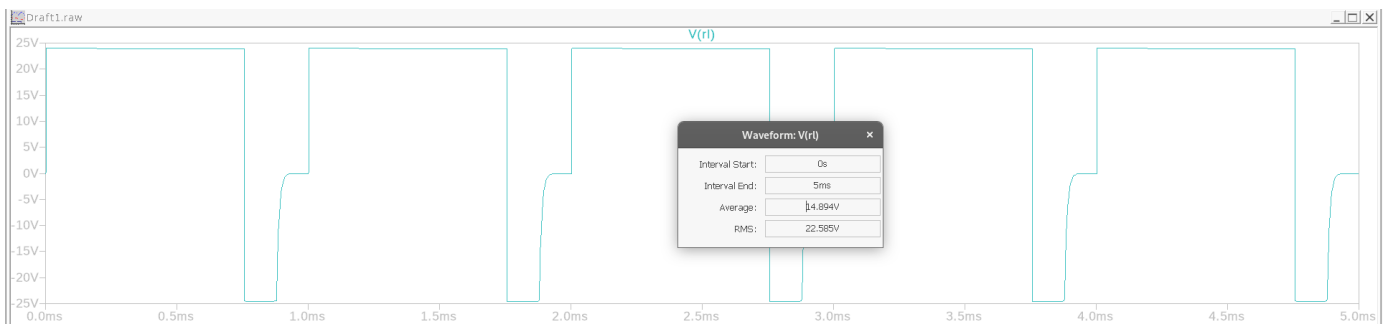


$D = 0.75$

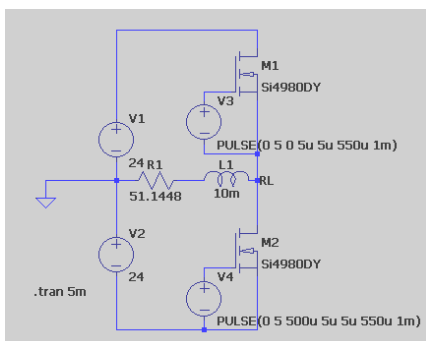
Question 6 - Bipolar switching RL load

$$R1 = \frac{511448}{10000} = 51.1448\Omega$$


Simulation done with $L = 10\text{m}$ instead of $L = 5\text{m}$, i compared my results with other people and there is not a big difference, the peaks are just more sharp.



$D = 0.55$

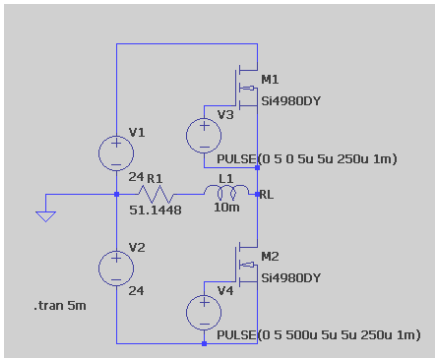


$D = 0.25$

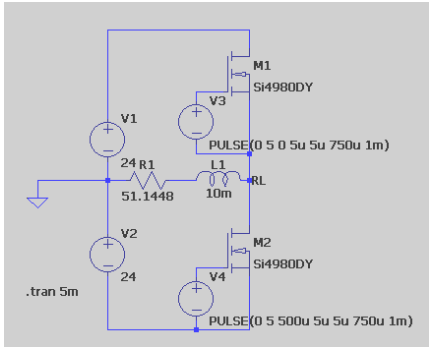


$D = 0.75$

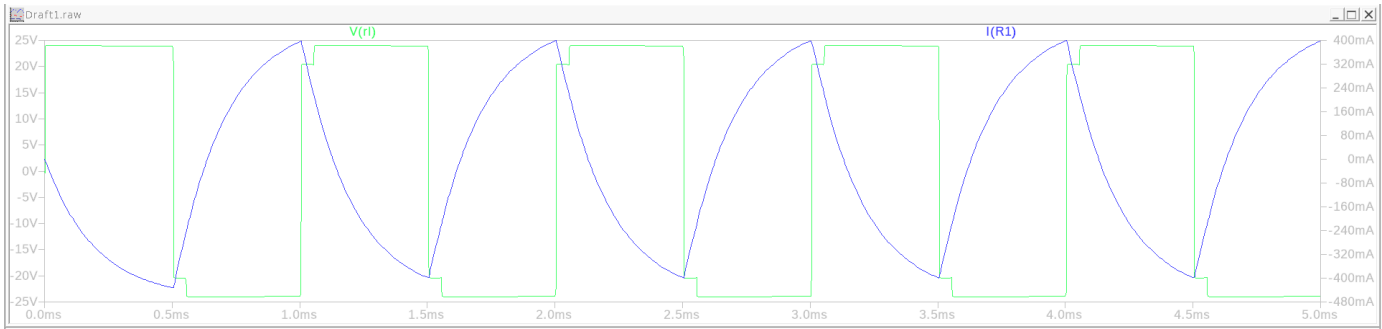
Show in a simulation the voltage across and current through the RL load.



$D = 0.55$

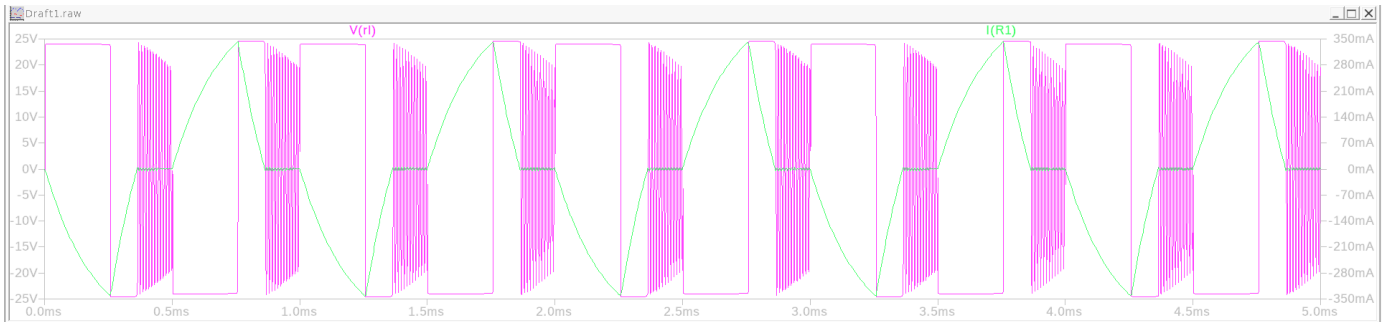


$D = 0.25$

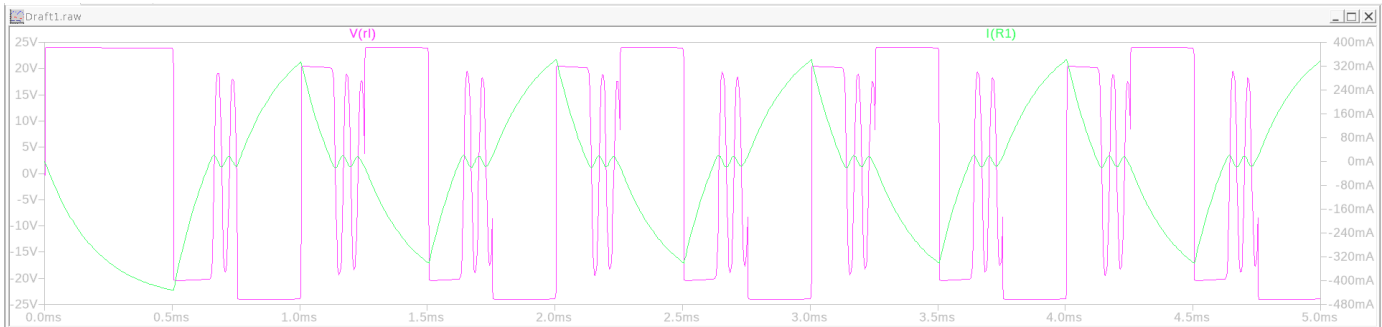


$D = 0.75$

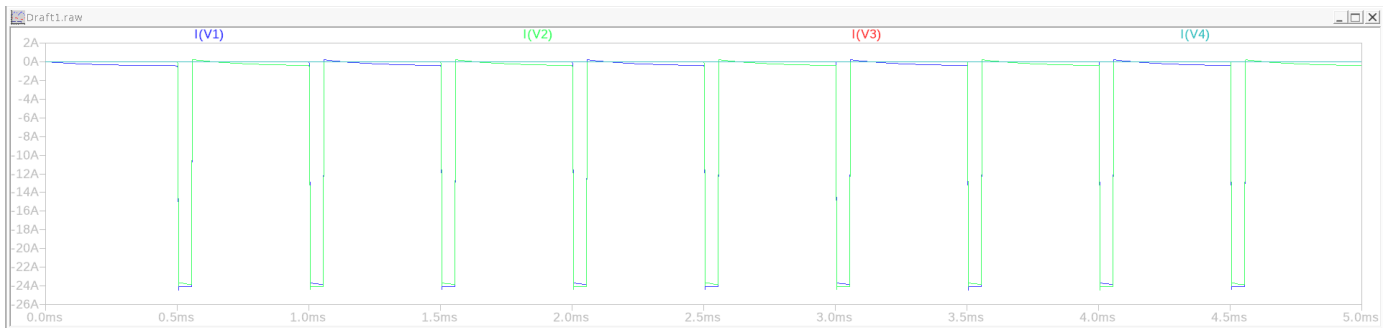
Show in a simulation the source currents.



$D = 0.55$

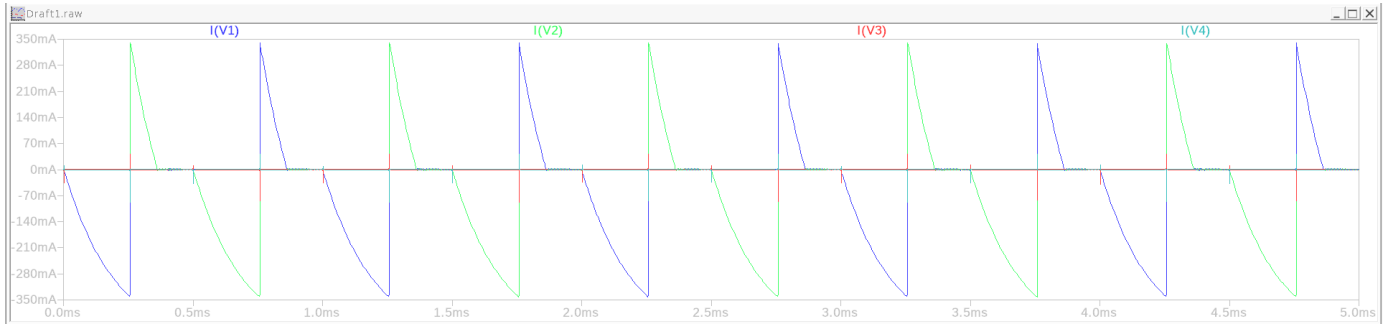

$D = 0.25$

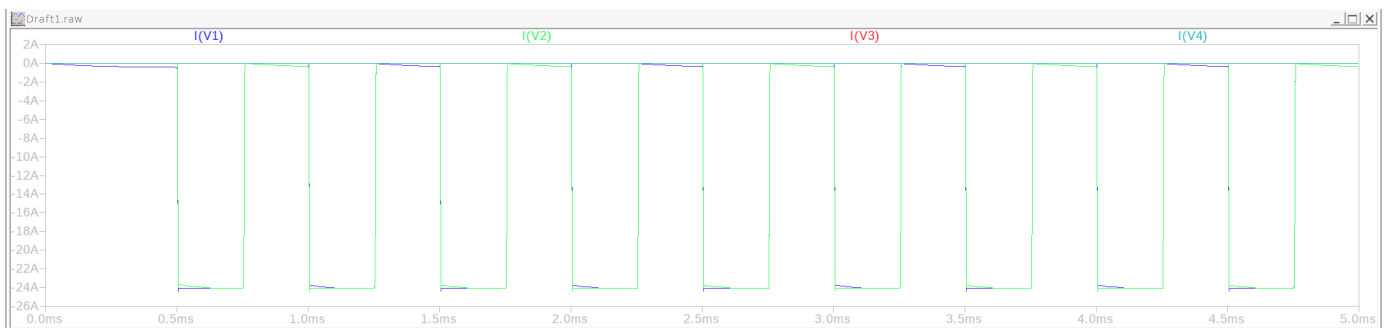


$D = 0.75$


What is the average voltage across the RL load?



$D = 0.55$

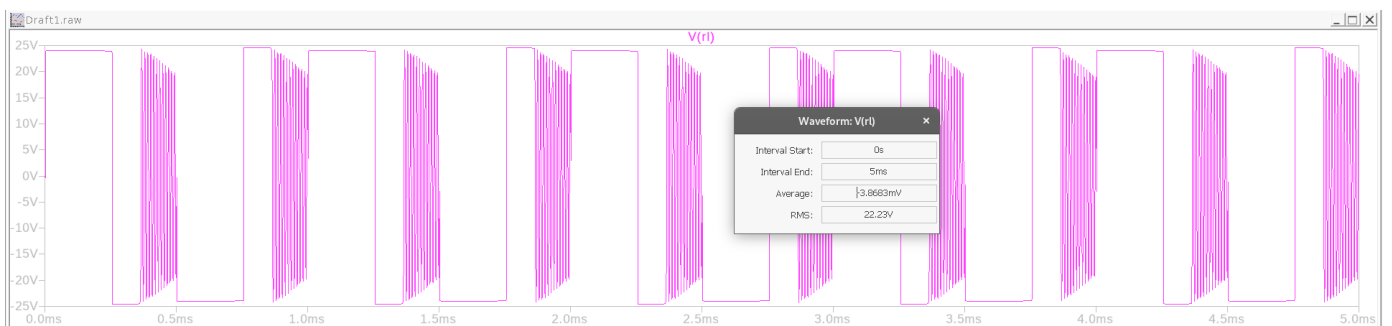


$D = 0.25$

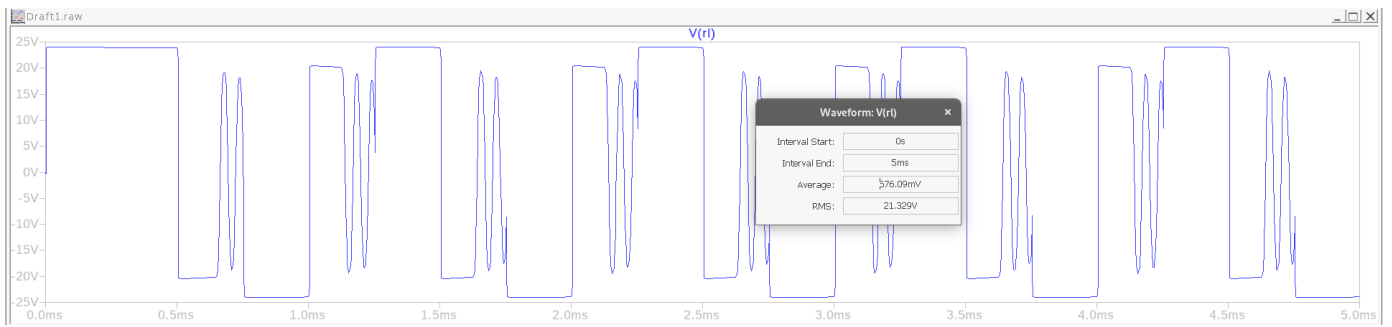


$D = 0.75$

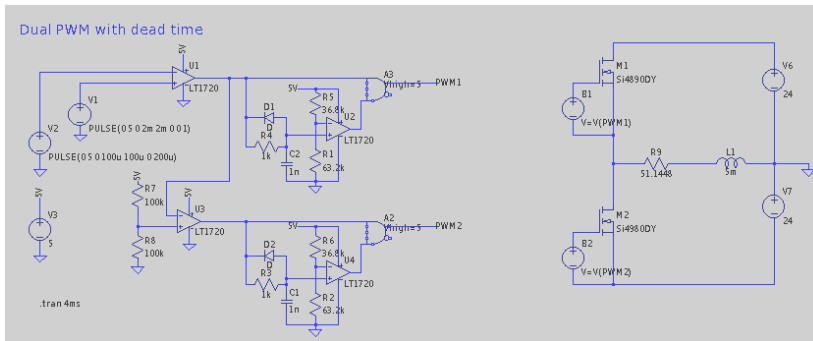Question 7 - PWM for half bridge



$$R1 = \frac{511448}{10000} = 51.1448\Omega$$




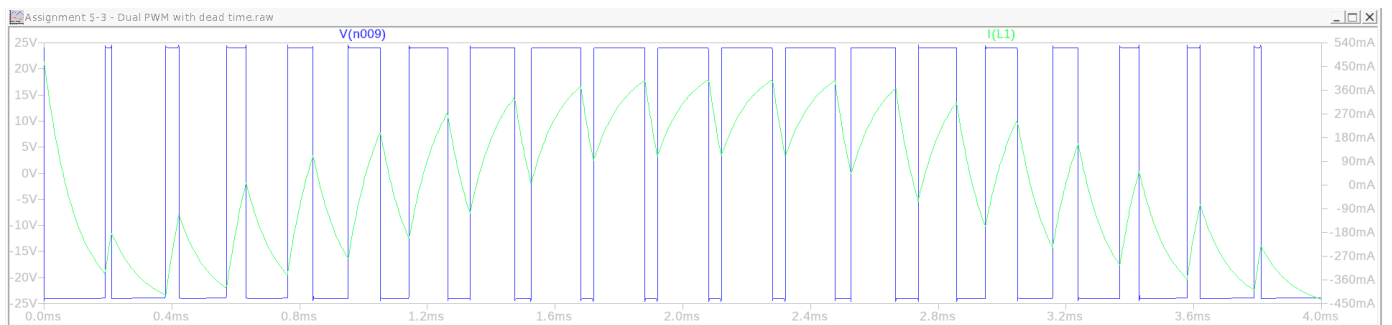
Show in a simulation the voltage across and current through the RL load.



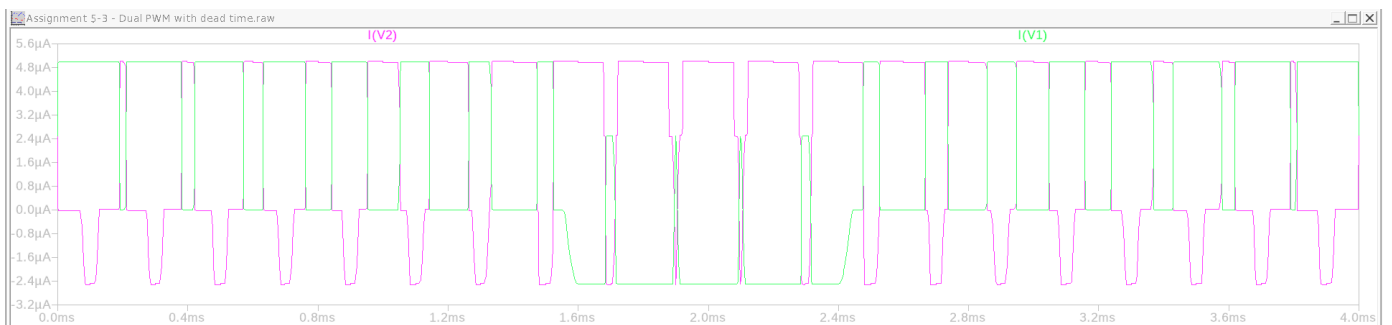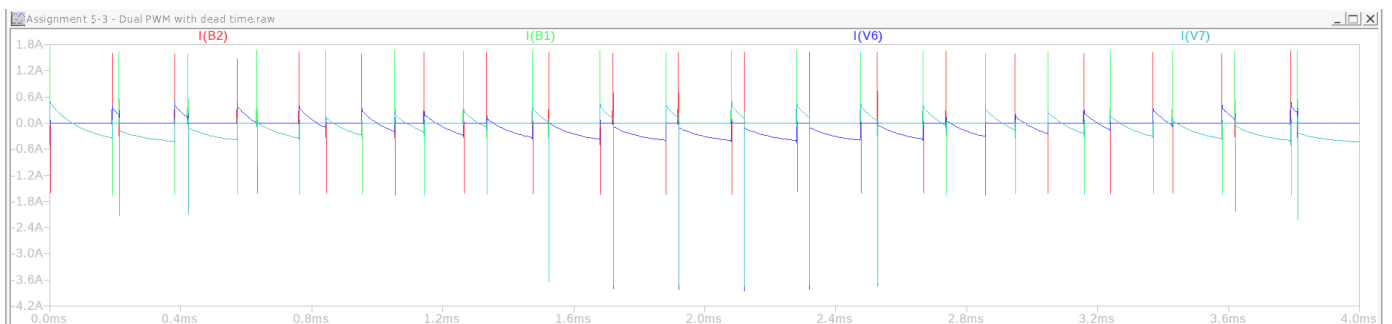Show in a simulation the source currents.



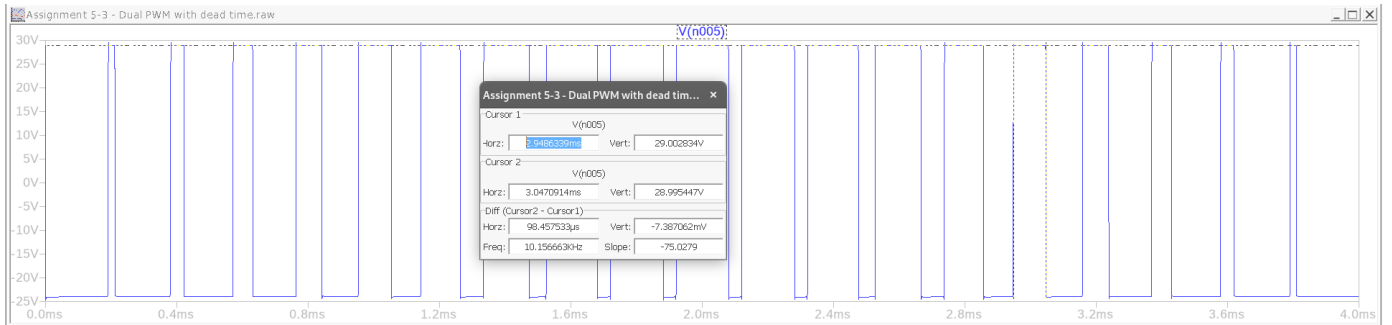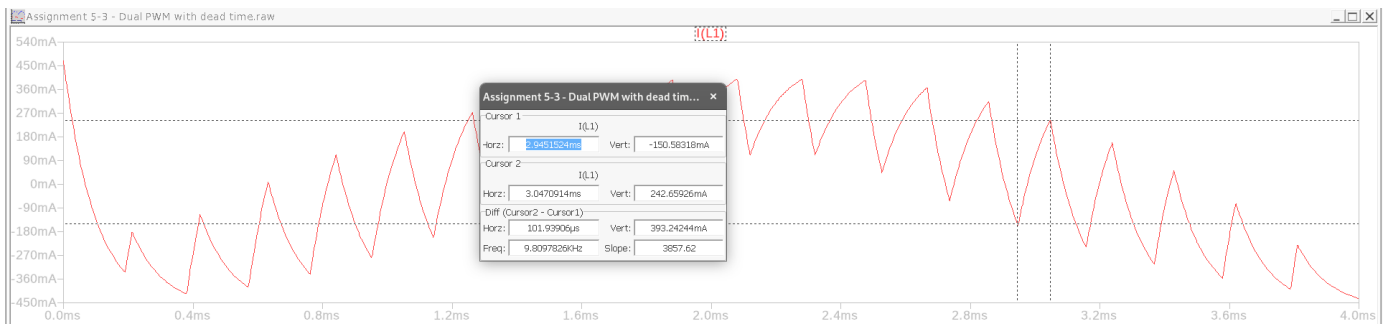For which duty cycle D there is the maximum ripple in the current?



The ripple current is the biggest at $t = 2.9ms$.

Since the duty cycle changes linearly and at $t = 2ms$, $D = 0.8$ and at $t = 4ms$, $D = 0$:

$$D = \frac{0.8}{(4-2)} \times (2.9 - 2) = 0.36$$

The ripple current is the biggest when $D \approx 0.36$